

# Mid Term Examination

Paper Code: ICT-103 (1<sup>st</sup> Sem)

Subject: Electrical Science

Time: 1:30 hrs

Max Marks: 30

Note: Attempt Q.No. 1 Which is compulsory and any two question from remaining.

Q.No.1

- a) Explain voltage and current divider rule with suitable example? Find the values of different voltages  $V_1$ ,  $V_2$  &  $V_3$  that can be obtained from a 12-V battery Fig.1. (4)

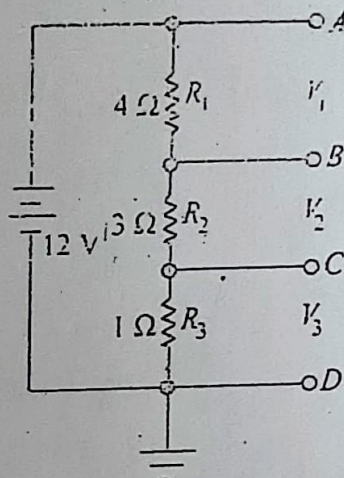


Fig.1

- b) In given circuit Fig. 2, calculate the values of (i)  $V_{AF}$  (ii)  $V_{EA}$  and (iii)  $V_{FB}$ . (3)

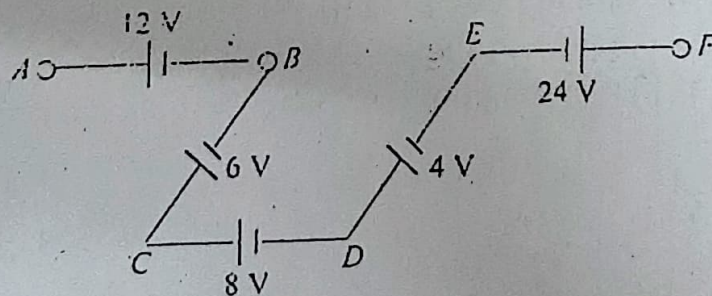


Fig.2

- c) Define Ohm's law, Kirchhoff's law with suitable example? (3)



**Q.No.2**

- a) State and explain Superposition theorem? Using Superposition theorem, find the current through the 40 ohm resistor of the circuit shown in Fig.3. All the resistances are in ohms.(8)

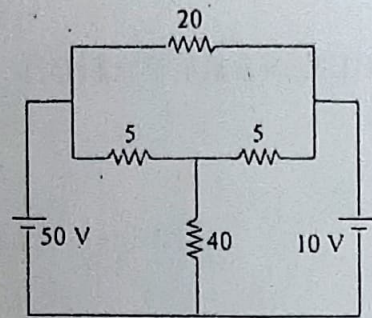


Fig.3

- b) Explain the source transformation with suitable example? (2)

**Q.No. 3**

- a) Derive the relationship to express three star connected resistances to equivalent delta? (5)
- b) Convert the circuit shown in Fig. 4, to a single voltage source in series with a single resistor. All the resistances are in ohm. (5)

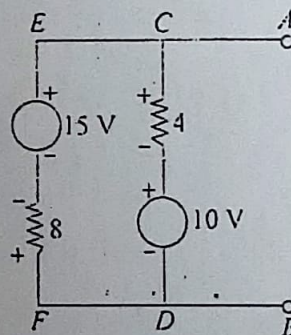


Fig.4

**Q.No.4**

- a) State and Explain Maximum Power Transfer Theorem? (4)
- b) For the circuit shown below in Fig.5, what will be the value of  $R_L$  to get the maximum power? What is the maximum power delivered to the load? (6)

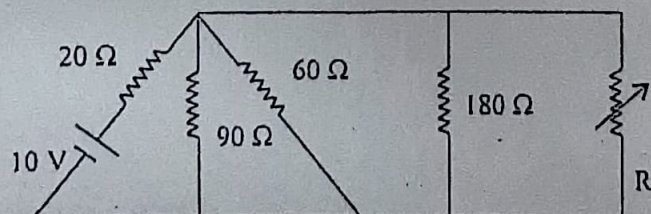


Fig.5